

<u>Integration Paper Circuit</u> Integrates the input signal.

 $V_{\text{out}} = -1/RC \int V_{\text{in}} dt$

Recommended values:

R1&R3: 10kΩ R2&R4: 1MΩ C#: 8nF

Try to use low tolerance/leakage for R1, R3, C1, and C2.

R2 and R4 are just to prevent drift in feedback capacitors. Choose a high value for these.

<u>Differentiation Paper Circuit</u> Differentiates the input signal.

 $V_{\text{out}} = -RC(dV_{\text{in}}/dt)$

Recommended values:

R1&R3: 1kΩ R2&R4: 100kΩ

C#: 1nF